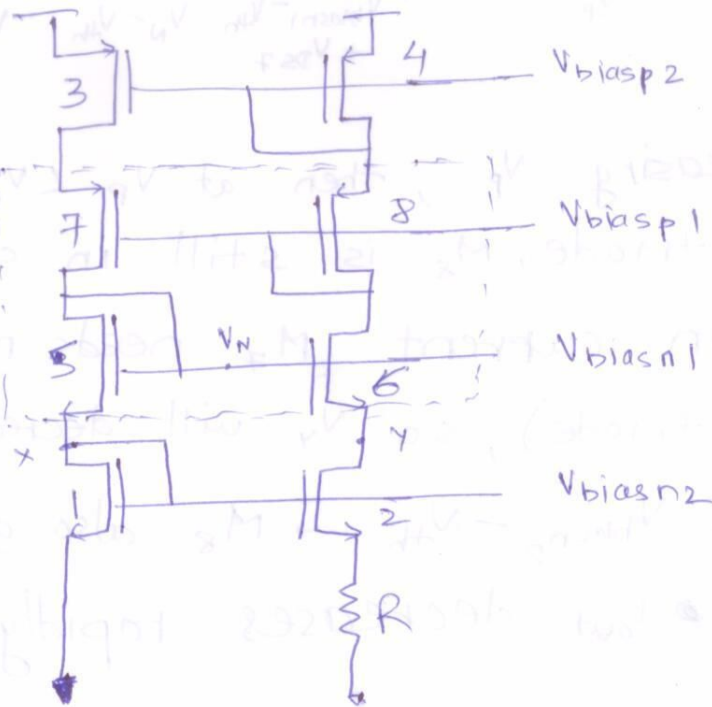


①

1. Simple cascode topology can be used.

→ Modification




$$V_x = V_N - V_{GS5}$$

$$V_y = V_N - V_{GS6}$$

$$\therefore V_x = V_y \rightarrow \text{channel length modulation}$$

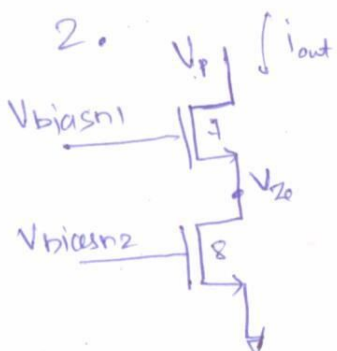$V_x = V_y \Rightarrow$ so same current through two branches.



If it is used to bias as shown in fig.

$$V_{P, \min} = V_{OV} + V_{2o}$$

$$= V_{OV} + V_y$$

$$= V_{OV} + V_x$$



$$= V_{OV} + V_{GS}$$

$$= V_{OV} + V_{GS} - V_{th} + V_{th}$$

$$= V_{OV} + V_{OV} + V_{th}$$

likel $\therefore V_{P,min} = 2V_{ov} + V_{th}$

①

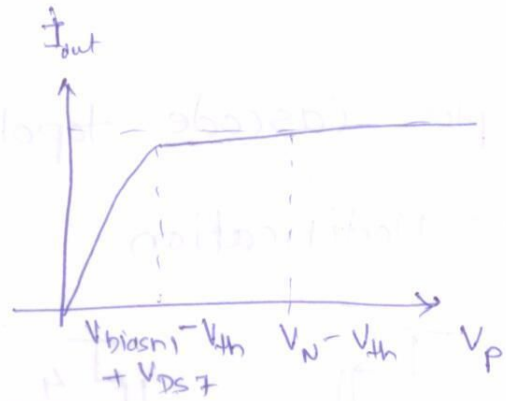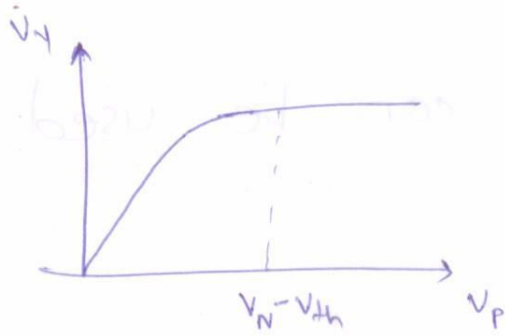

If we keep decreasing V_P , then at $V_P < V_N - V_{th}$ M_7 will go to triode, M_8 is still in sat. But to maintain current M_7 needs more V_{gs} (as it is in triode), so V_y will decrease. Eventually $V_y < V_{biasn2} - V_{th} \rightarrow M_8$ also goes to ~~sat~~ triode and I_{out} decreases rapidly.

low voltage

2. OP-AMP design.


(2) ~~(1)~~

Distributing currents as,

Bias circuit = $200 \mu A$

Differential pair = $800 \mu A$

CS stage = $1 mA$

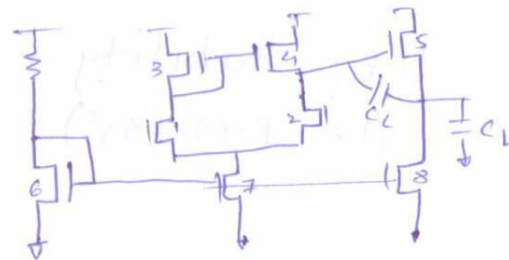

Also, $g_{m1} = g_{m5} = 1m$ (assuming)

$$\therefore g_{m5} = \sqrt{2\beta_5 I_D}$$

$$\left(\frac{W}{L}\right)_5 = 12.5$$

$$I_{D1} = I_{D2} = \frac{800 \mu A}{2} = 400 \mu A$$

$$\therefore \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 10.41$$

$$r_{on2} = \frac{1}{\lambda_n I_{D2}} = \frac{1}{0.01 \times 0.4m} = 250 K$$

$$r_{op4} = \frac{1}{\lambda_p I_{D4}} = \frac{1}{0.0125 \times 0.4m} = 200 K$$

$$R_{out1} = r_{on1} \parallel r_{op4} = 111 K$$

$$r_{on8} = \frac{1}{\lambda_n I_{D8}} = \frac{1}{0.01 \times 1m} = 100 K$$

$$r_{op5} = \frac{1}{\lambda_p I_{D5}} = \frac{1}{0.0125 \times 1m} = 80 K$$

$$R_{out2} = 44 K$$

$$\text{dc Gain} = g_{m1} \cdot g_{m2} R_{out1} \cdot R_{out2}$$

$$\boxed{\text{Gain} = 4884}$$

For stability, $\omega_{P2} = \frac{g_{m5}}{C_L} \geq \omega_{unity} = \frac{g_{m1}}{C_C}$
(i.e. P.M. = 45°)

$$g_{m5} = g_{m1}$$

$$\therefore C_C \geq C_L$$

$$\therefore C_C \geq 1.5p$$

$$\therefore \text{Choosing } \boxed{C_C = 2pF}$$

$$\therefore \omega_{unity} = \frac{g_{m1}}{C_C} = 500 \text{ MHz}$$

$$\omega_{-3} = \frac{1}{R_{out1} (1 + g_{m5} R_{out2}) \cdot C_C}$$

$$\boxed{\omega_{-3} = 100.100 \text{ KHz}}$$

$$V_{ov5} = \frac{g_{m5}}{\beta} = \frac{I_m}{\mu_P \left(\frac{W}{L} \right)_5} = 2$$

CM for M_5 comes from first stage.

$$\therefore \text{Same } V_{thp} + V_{ov5} = V_{ov4} = V_{GS4} - V_{th} = V_{GS3}$$

$$\therefore I_{D3} = 0.4 \text{ m} = \frac{1}{2} \beta_{P3} (V_{GS3} - V_{thp})^2$$

$$\boxed{\begin{array}{l} \left(\frac{W}{L} \right)_3 = 5 \\ \left(\frac{W}{L} \right)_4 = 5 \end{array}}$$

$$I_{bias} = \frac{1}{2} \times \beta_6 (V_{ov6})^2 = 200 \mu A$$

$$V_{ov6} = V_{ov7} = V_{ov8}$$

3

$$\therefore \left(\frac{W}{L}\right)_6 = 3.33$$

$$\text{for, } I_{diff-pair} = 0.8 \text{ mA}, \quad \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_6 \times \frac{0.8}{0.2}$$

$$\boxed{\left(\frac{W}{L}\right)_7 = 13.33}$$

$$\text{for } I_{cs} = 1 \text{ mA} \quad \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_6 \times \frac{1 \text{ m}}{0.2 \text{ m}} =$$

$$\boxed{\left(\frac{W}{L}\right)_8 = 16.16}$$

$$V_{swing \text{ at } CS} = 3 - (2 + 1) = 2 \text{ V}$$

$$V_{GS,6} = 1 + 0.8 = 1.8$$

$$\therefore 5 - IR = V_{GS,6}$$

$$\boxed{\therefore R = 16 \text{ K}}$$

Performance obtained, \rightarrow

$$\text{Gain} = 73 \text{ dB}$$

$$\omega_{-3} = 100.100 \text{ KHz}$$

$$\omega_{unity} = 500 \text{ MHz}$$

$$P_{diss} = 10 \text{ mW}$$

$$C_c = 2 \text{ pF}$$

$$R = 16 \text{ K}\Omega$$

$$C_{L(max)} = 1.5 \text{ pF}$$

sizings, are

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 10.41$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 2.37$$

$$\left(\frac{W}{L}\right)_5 = 12.5$$

$$\left(\frac{W}{L}\right)_6 = 3.33$$

$$\left(\frac{W}{L}\right)_7 = 13.33$$

$$\left(\frac{W}{L}\right)_8 = 16.16$$

~~V_{ov} remaining for M₇ assuming~~

$$V_{ov2} = \frac{g_{m2}}{\beta_2} = \frac{1\text{m}}{120\mu \times 10.41} = 0.8\text{V}$$

Assuming swing requirement at stage 1 is

$$|V_{GS5}| = V_{OV5} + |V_{thP}|$$

$$= V_{OV4}$$

$$= |V_{GS4}| - |V_{thP}|$$

$$= |V_{GS3}| - |V_{thP}|$$

$$= V_{OV3}$$

$$= 2 + 0.9$$

$$V_{OV3} = 2.9\text{V}$$

$$I_{D3} = 0.4\text{m} = \frac{1}{2} \times 40\mu \left(\frac{W}{L}\right)_3 (V_{OV3})^2$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 2.37$$

$$\therefore V_{OV4} = 2.9$$

$$V_{OV2} = \frac{g_{m2}}{\beta_2} = \frac{1\text{m}}{120\mu \times (10.41)} = 0.8$$

Assuming swing requirement at stage 1 = 0.3V

\therefore V_{ov} remaining for M₇,

$$V_{OV7} = 5 - (2.9 + 0.8 + 0.3)$$

$$V_{OV7} = 1\text{V}$$

Note that the design has been optimized for performance, not for power dissipation. Also ⁽⁴⁾ all the parameters required are within specified limit.

Also swing at both the stages is ~~finite~~ valid. It is necessary to check this because $g_{m1} \neq g_{m2}$ ~~was~~ were assumed.