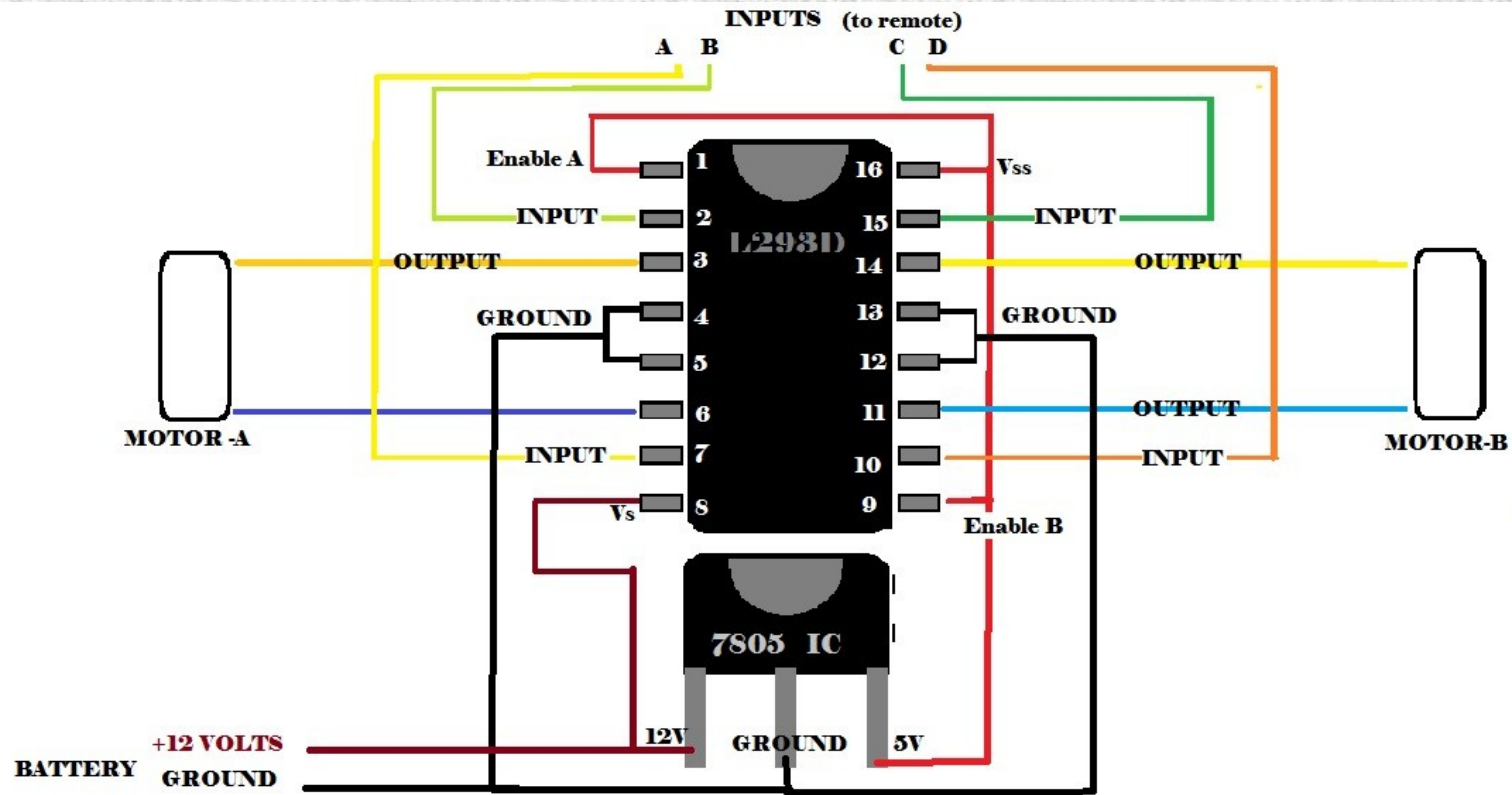


XLR8

Electrical Session


Learn to make the brain of your



By
-Robotics club

How to run the motors??


4 motors using just 1 remote !!

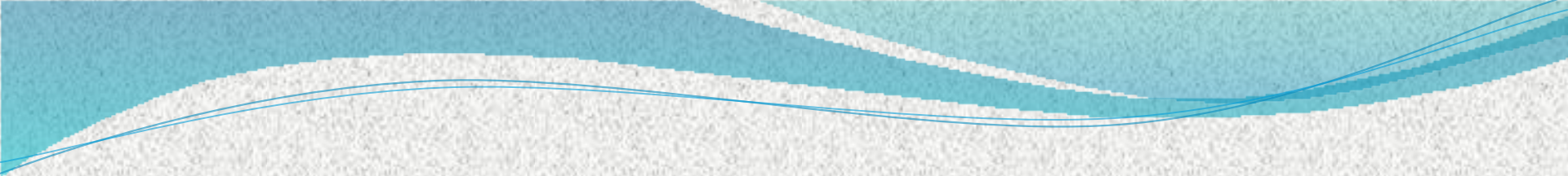

**Let's start with something
useful and simple....**


H bridge

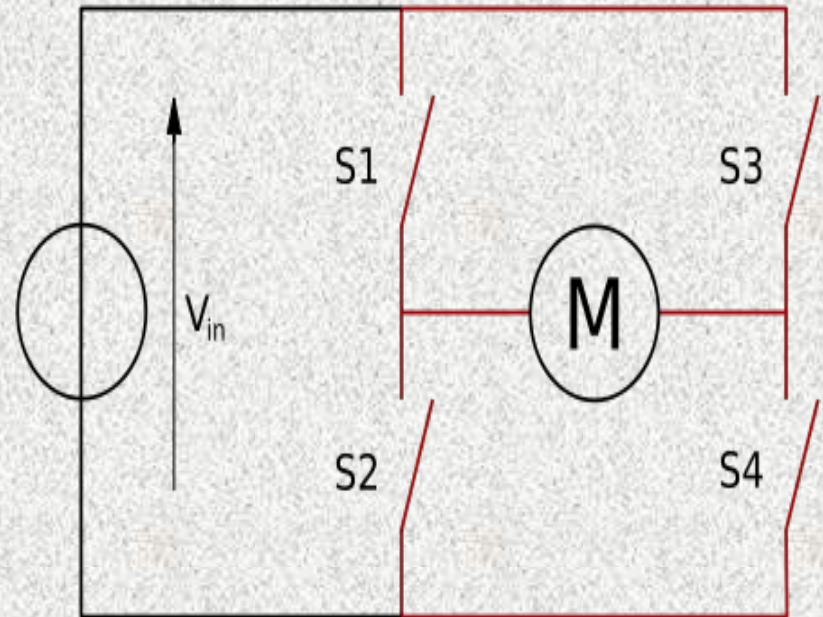- An **H bridge** is an **electronic circuit** that enables a voltage to be applied across a load in either direction.
- See it for yourself in which direction current goes when S1 and S4 are on and when S2 and S3 are on.
- Using such a circuit, you can supply current to the motor in two directions!!!!



Make your own Remote-DPDT Switches

- 2 DPDT switches used for 2 Motor each.

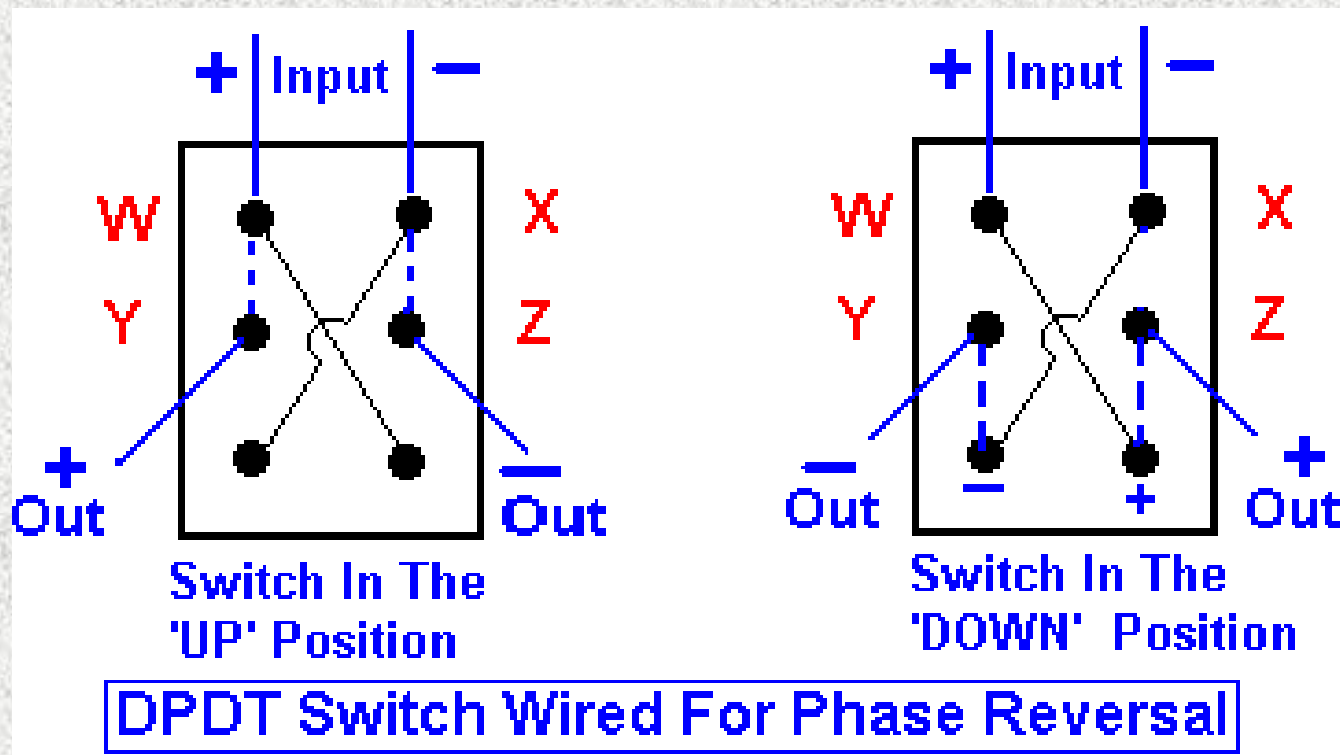



Our Main task is to build a circuit that will enable us to drive the motors through switches wirelessly.


For this we would need some Electrical Components

- **RF Circuit:** A Circuit to enable the wireless communication between our Remote and the car
- **L293D IC:** Something to drive the motor as per command

As we would see the above components would work only in some specific voltage range, we would need to build a circuit to convert the DC voltage from a battery to the voltage in specific range


Radio Frequency Circuit (RF Circuit)

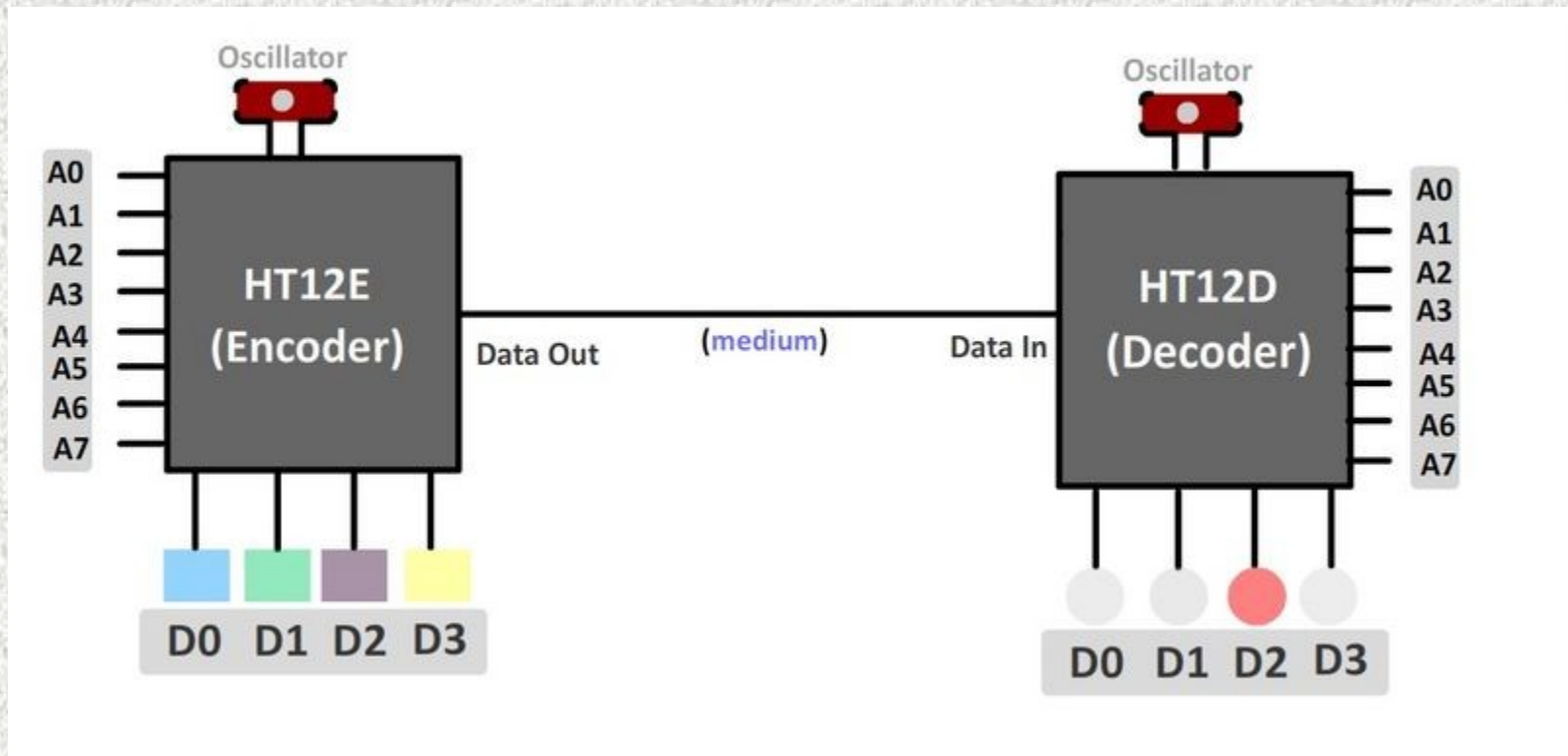- Used in remote controlled robots and implements wireless communication.



How it works???

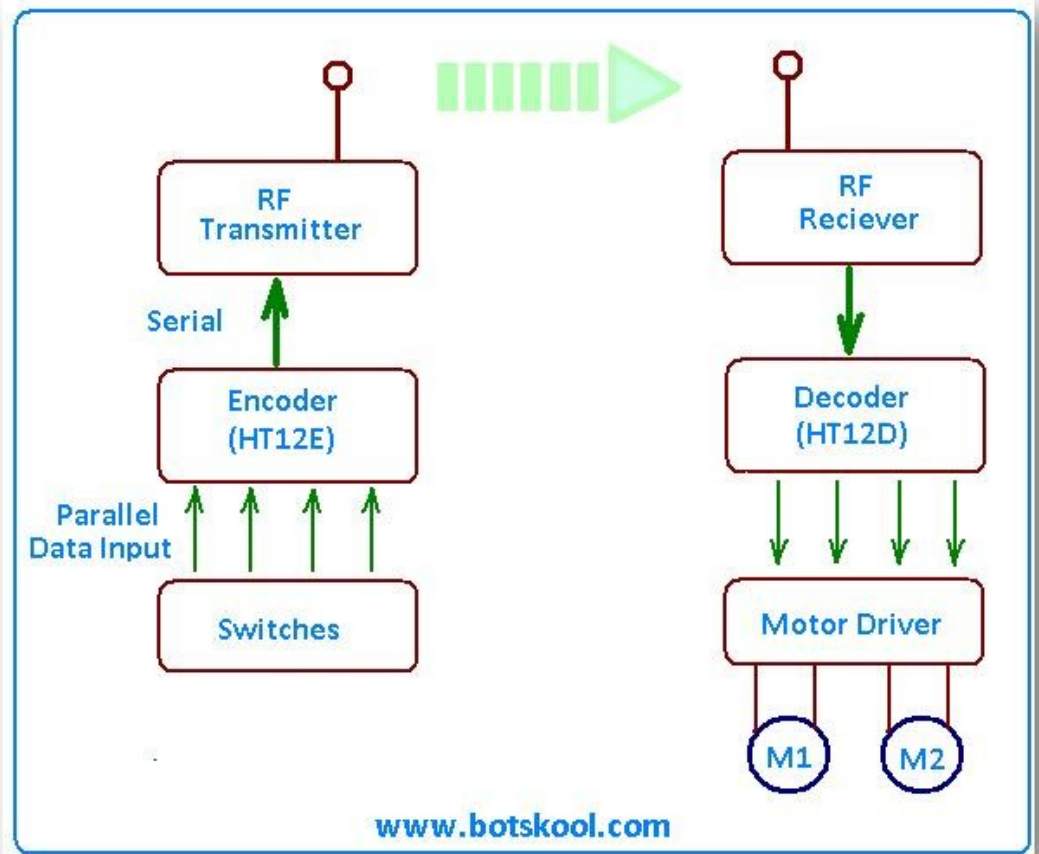- Your input is 4 lows/highs in terms of voltage.
- Input is encoded sent to the transmitter.
- Signal is received by the receiver and decoded.
- This input is then sent to Motor driver (here L293D)
- More about L293d to come in few minutes!!!
- L293D drives the motor according to the input.



How to implement it??

- Connect the input from DPDT switches to channels in the encoder circuit.

Input (from
DPDT
switches)



Transceiver



- Connect the output pins in decoder circuit to corresponding pins of the Receiver

1293D




Receiver

Interference due to Same Frequency


- **Solution is simple:**
Change your address bits (both in Encoder and Decoder)
- **Two Encoder and Decoders talk to each other only if they have same address bit combination.**
- **Your address bit combination is like your password!!!**

**8-Address
4-Address/Data**

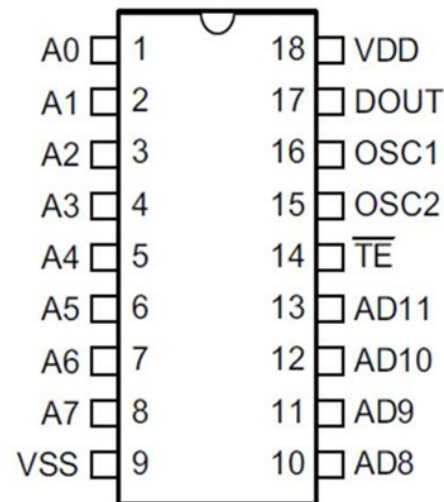

**HT12E
- 18 DIP**


**8-Address
4-Data**

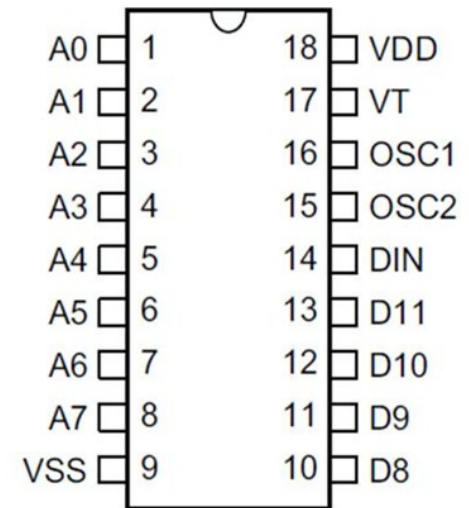

**HT12D
- 18 DIP-A**

7805 IC

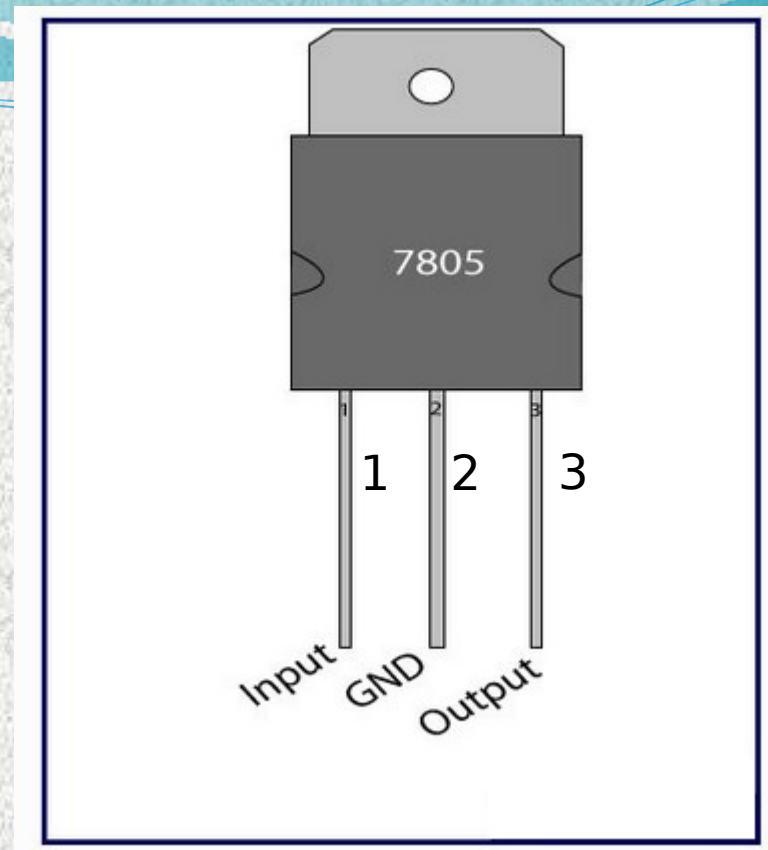- Three terminal positive voltage regulator.
- It is used to convert 12V supplied by the battery to 5V.
- **Don't forget to attach heat sink** as remaining voltage is wasted as heat.
- Very important component in a circuit as all RF circuits (to be introduced after few slides) and sensors work on



Pin No	Function	Name
1	Input voltage (5V-18V)	Input
2	Ground (0V)	Ground
3	Regulated output; 5V (4.8V-5.2V)	Output






As we would see later our car would receives a signal of only of 5 volts or less than 5volts.

But our motor needs around $> 9V$ to run and about 12 V to run efficiently.
So how do we run motors of 12 Volts???


We need a circuit that acts as a switch
i.e. when it gets 5volt signal it switches 12 volts
to the motors.


L293D – Motor Driver IC

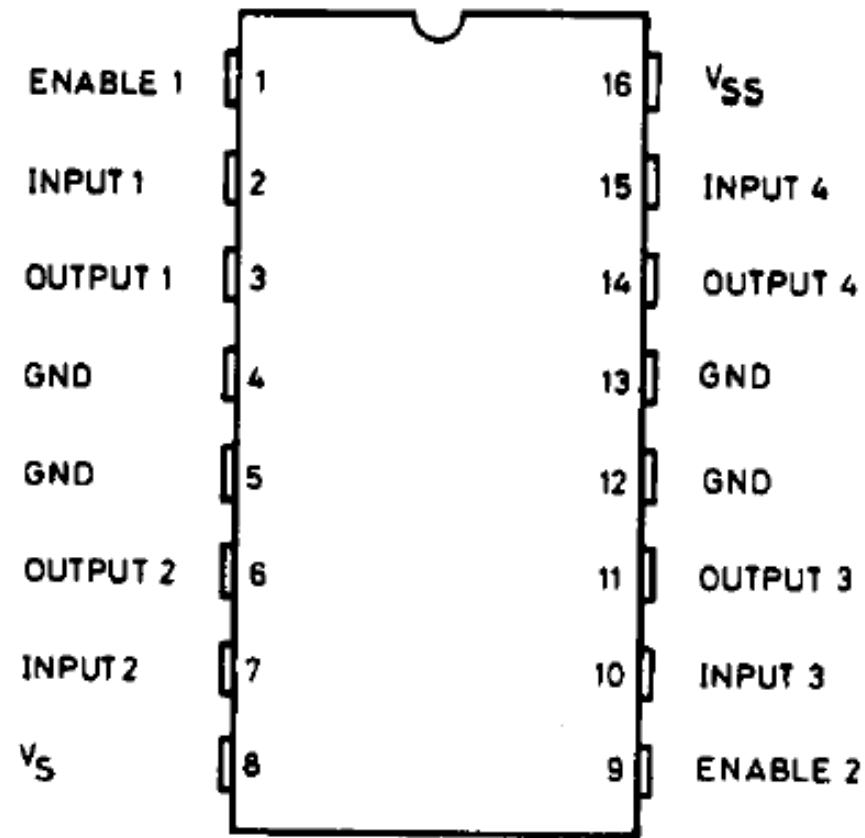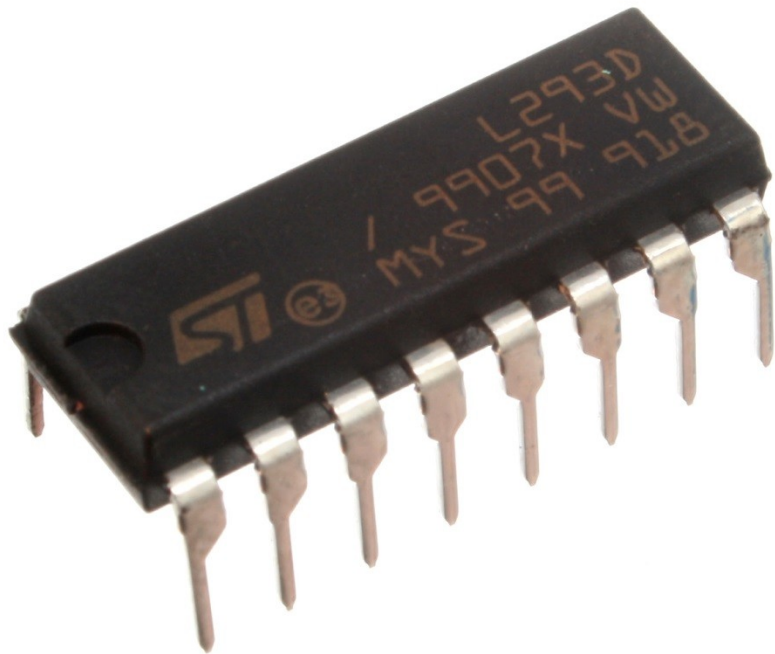

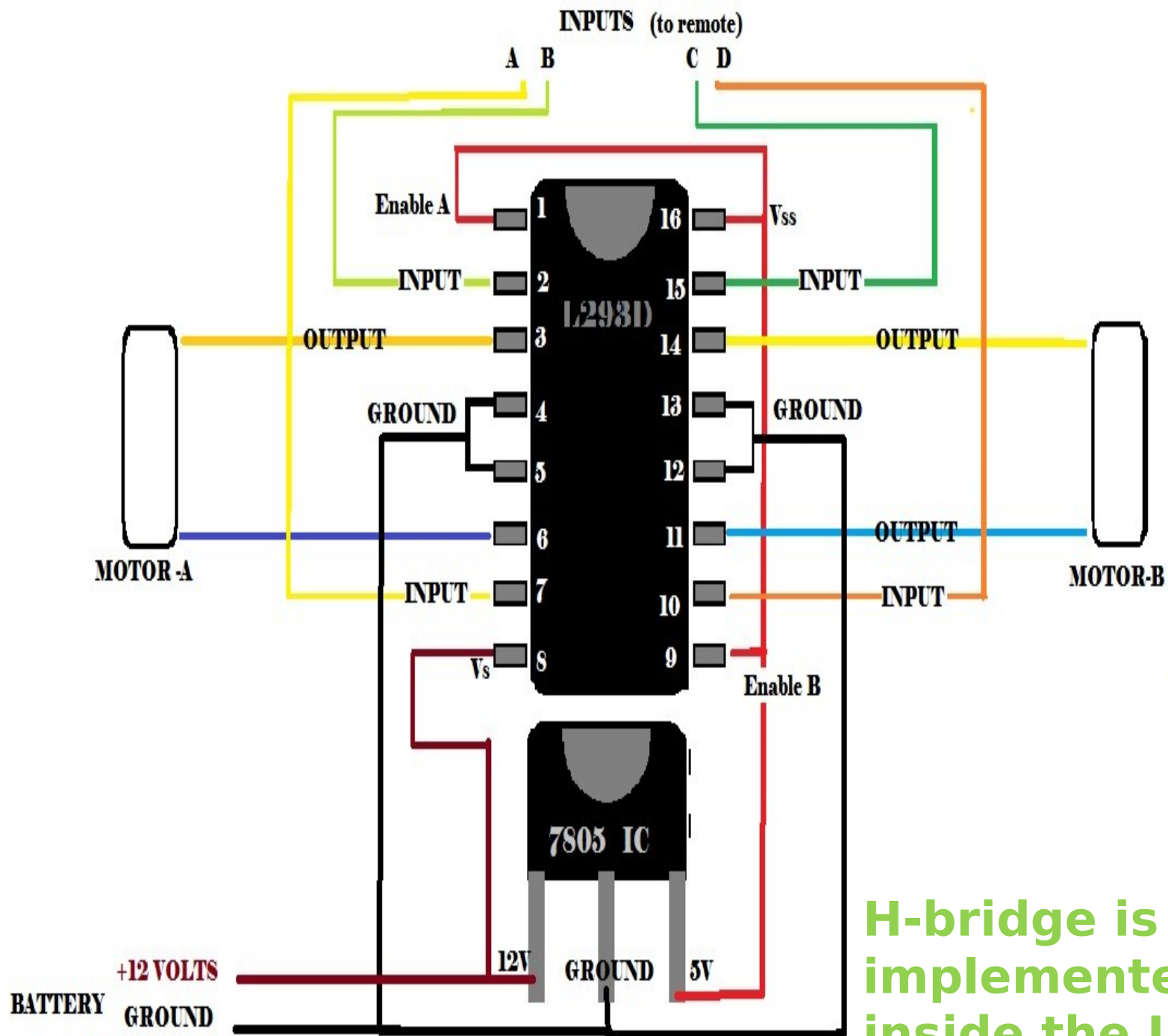

H-bridge is implemented inside the L293D

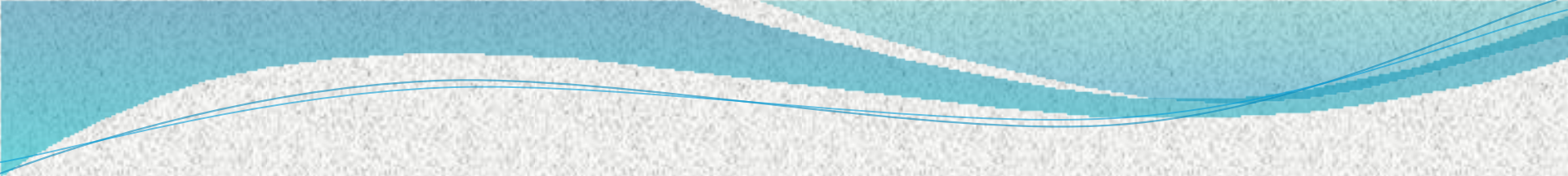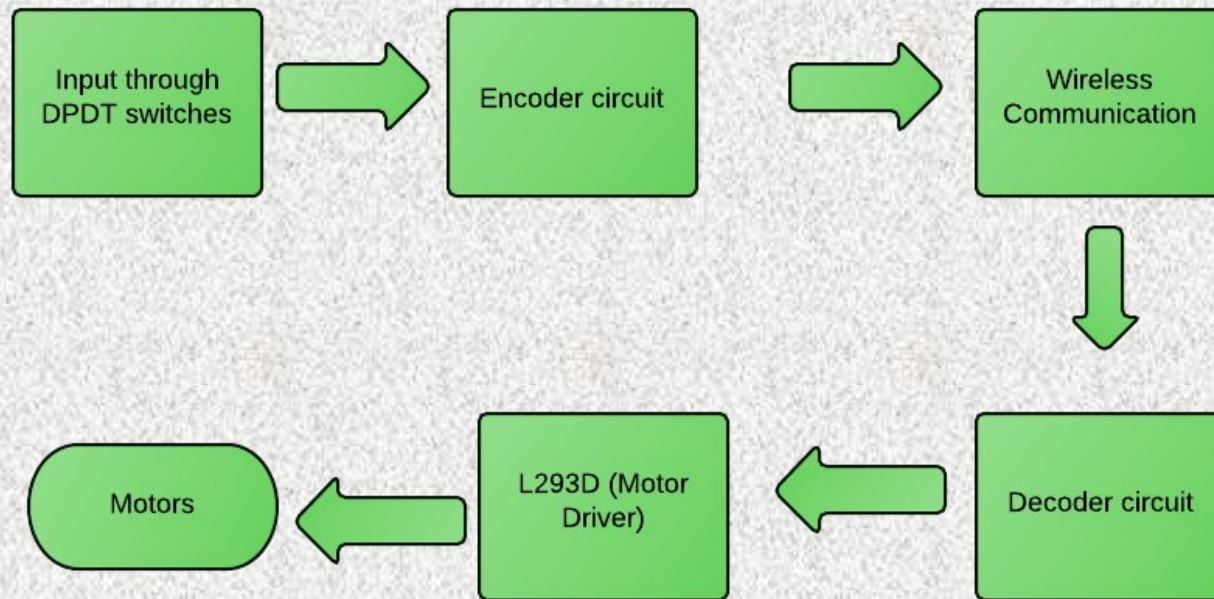
- 
- When a button is pressed the information is encoded and converted into a signal.
 - The transmitter sends a signal in the range 5 volts.
 - At the Receiver the voltage signal gets decoded again , and the information is received.
 - The output from the receiver is also of 5V finally.



We have our answers
now ☐☐



Any Doubts ???



Thanks !!
And Keep up the Enthu!!

Yash: 9967164641

Riddhish: 9769472731

Rishabh: 9892314375

Ankita: 9773619340